

3 (Sem-5) ELE M 5

2016

ELECTRONICS

(Major)

Paper : 5.5

(Network Analysis)

Full Marks : 60

Time : 3 hours

*The figures in the margin indicate full marks
for the questions*

1. Give objective-type answer to the following : 1×7=7
- (a) How can we define a distributed element?
 - (b) What do you mean by a constant voltage source?
 - (c) Define graph of a network.
 - (d) Write an expression for power dissipated in an inductor.
 - (e) Give the expression for Laplace transform of $\sin at$.
 - (f) Write the expression for Fourier coefficient a_n .
 - (g) What is band elimination filter?

A7/132

(Turn Over)


(2)

2. Give short answer to the following (any four) :
2×4=8

- (a) Define node and mesh of a network.
- (b) Define Laplace transform of a unit step function.
- (c) How can we define the poles and zeros of a network function?
- (d) What is the quality factor of an $R-L-C$ network?
- (e) What is passive filter?

3. Write short answer to any three of the following :
5×3=15

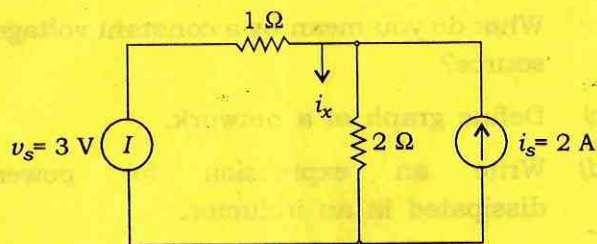- (a) For the circuit given below, calculate the branch current i_x :



- (b) Evaluate the Laplace transform of the following :

- (i) $\sin at$
- (ii) $\int f(t) dt$

(3)

- (c) State and prove the maximum power transfer theorem.

- (d) Draw the circuit diagram of a first-order Butterworth filter and discuss briefly about the circuit.

- (e) Discuss briefly about the significance of network functions.

4. Answer any three of the following : 10×3=30

- (a) Derive the open circuit impedance parameter of a two-port network.

- (b) Synthesize the one-port $L-C$ network using Foster's second form of equivalent network and evaluate the elements of the network.

- (c) For a π -section filter, show that the characteristics impedance is given by

$$Z_{0\pi} = \frac{Z_1 Z_2}{Z_{0T}}$$

where the symbols have their usual meanings.

- (d) Write short notes on the following :

- (i) m -derived filter
- (ii) Routh-Hurwitz stability criteria
